
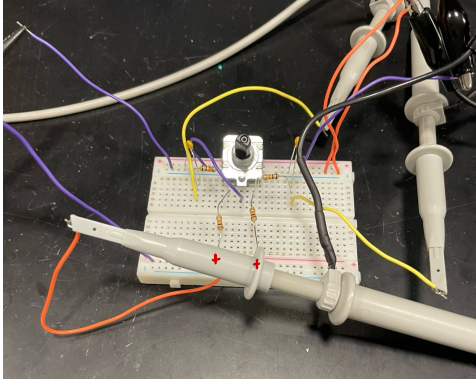


03/08/2025

Rotary encoder functionality test

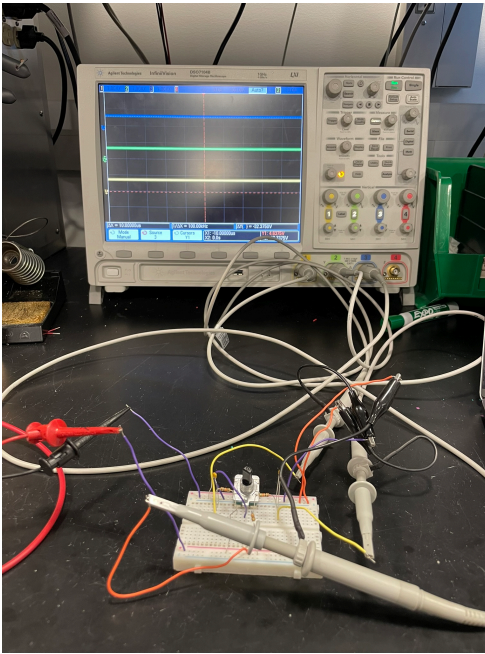

resistors: $10\text{ k}\Omega$
capacitors: $0.01\mu\text{F}$
supply voltage: $+5\text{ V DC}$



channel 1: RotA

channel 2: RotB

channel 3: supply voltage



clockwise rotation



counterclockwise rotation

Rotary encoder code

set interrupt on RotB GPIO

if $A=0 + B=0$, clockwise


if $A=1 + B=0$, counterclockwise

if $A=1 + B=1$, no change


LEDs functionality test

resistors: 100Ω


voltage supply: 2.6V DC

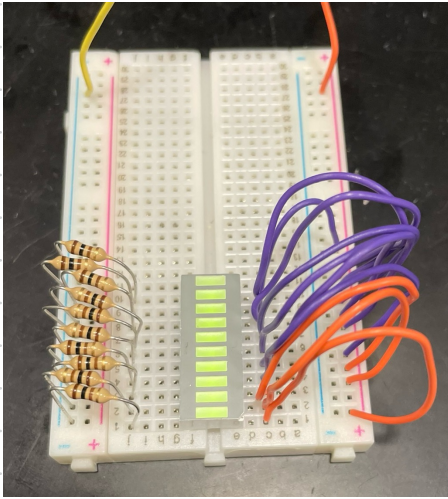

✓ green LEDs functional
LTA-1000G

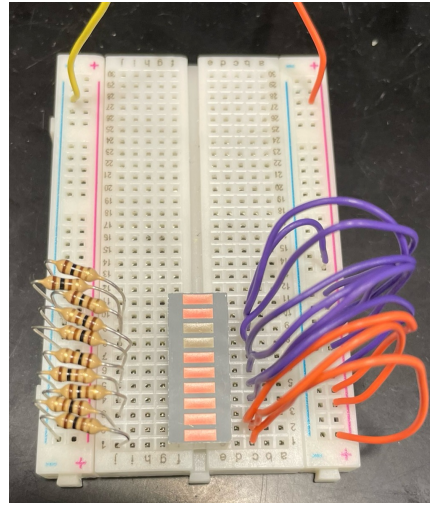


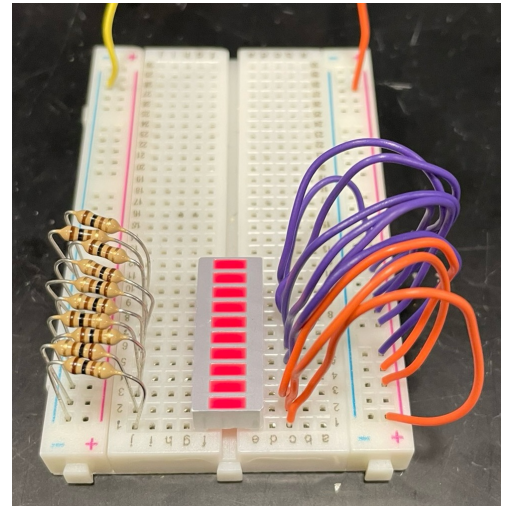✗ DC10EWA not functional
two LEDs not working



✓ red LEDs functional

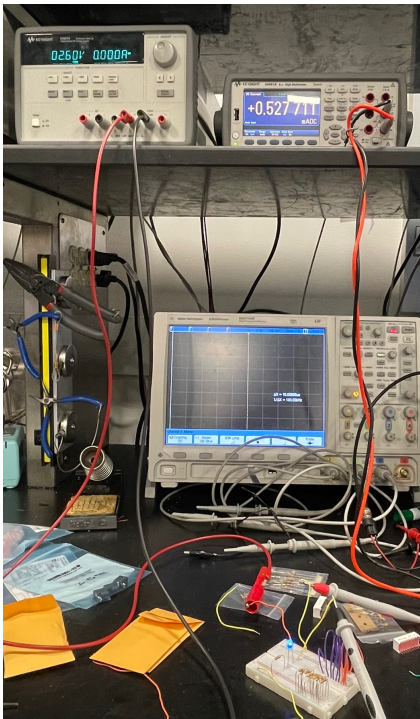★ need yellow array of LEDs to be ordered



blue LED lit at 2.6V + 0.528 mA

this is approximately the GPIO output voltage